

Problem: the circuit operates at steady-state. Find the expression of $v_1(t)$, $i_2(t)$.
Data: $v_{S1}(t) = \sin(3t - 135^\circ)$ V.

